 



[1. Full Adder]



$$\text{Sum, } S = A \oplus B \oplus C_{in}$$

$$\text{Carry, } C_{out} = Ab + AC_{in} + BC_{in}$$

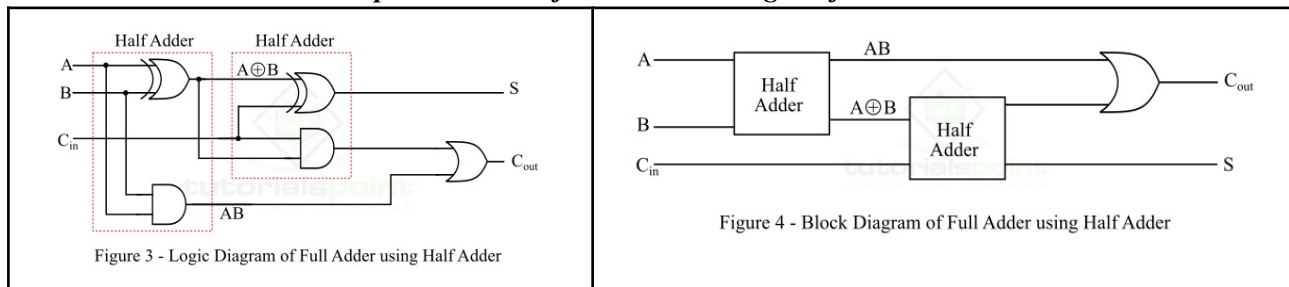Implementation of Full Adder using Half Adder



RTL

```
// =====
// Full Adder Module 2 (using 2 Half Adders)
// This module implements a full adder using two half adder instances,
// taking three 1-bit bin inputs (a, b, cin) and producing a 1-bit sum and cout.
// =====
module full_adder(a, b, cin, sum, cout);
    input a, b, cin; // Input: a (First input bit), b (Second input bit), cin (Carry-in input)
    output sum, cout; // Output: sum (Final sum), cout (Final carry-out)

    wire I1, I2, I3; // Intermediate wires: I1 (sum from ha1), I2 (carry from ha1), I3 (carry from ha2)

    // Instantiate first Half Adder for a and b
    half_adder ha1(.A(a), .B(b), .S(I1), .C(I2));
    // Instantiate second Half Adder for I1 and cin
    half_adder ha2(.A(I1), .B(cin), .S(sum), .C(I3));

    // Final carry-out is OR of both carries
    assign cout = I2 | I3;
endmodule

// =====
// Half Adder Module
// This module performs the basic half-adder logic,
// which computes the sum and carry-out of two 1-bit binary inputs.
// =====
module half_adder (A, B, S, C);
    input A,B; // A: First input bit, B: Second input bit
    output S,C; // S(sum): XOR of A and B, C(carry-out): AND of A and B

    // Logic for sum and carry
    assign {C, S} = {A & B, A ^ B};
endmodule
```

```
endmodule
```

```
// =====  
// Full Adder Module 2  
// This module implements a full adder using two half adder instances,  
// taking three 1-bit bin inputs (a, b, cin) and producing a 1-bit sum and cout.  
// =====  
module full_adder (a, b, cin, sum, cout);  
    input a, b, cin;    // Input: a (First input bit), b (Second input bit), cin (Carry-in input)  
    output sum, cout;    // Output: sum (Final sum), cout (Final carry-out)  
  
    // Logic for sum and carry  
    // assign {cout, sum} = a + b + cin;  
    // assign {cout, sum} = {((a & b) | (b & cin) | (a & cin)), (a ^ b ^ cin)};  
    assign sum = a ^ b ^ cin;  
    assign cout = (a & b) | (b & cin) | (cin & a);  
endmodule
```

TB

```
// =====  
// Testbench for Full Adder Module  
// This testbench verifies the behavior of the full_adder module  
// by applying all possible 1-bit input combinations (2^3 = 8 cases) and monitoring outputs.  
// =====  
module tb_full_adder;  
    reg net_test_a;    // Input a for testing: First input bit  
    reg net_test_b;    // Input b for testing: Second input bit  
    reg net_test_cin;  // Input cin for testing: Carry-in bit  
    wire net_test_sum; // Output sum for testing: Result of the addition  
    wire net_test_cout; // Output cout for testing: Carry-out bit  
  
    // Instantiate Full Adder module  
    full_adder fa_test (  
        .a(net_test_a),    // Connect test input a to module input a  
        .b(net_test_b),    // Connect test input b to module input b  
        .cin(net_test_cin), // Connect test input cin to module input cin  
        .sum(net_test_sum), // Connect module output sum to test wire  
        .cout(net_test_cout) // Connect module output cout to test wire  
    );  
  
    // Initial block to perform test cases  
    initial begin  
        // Create VCD file for waveform analysis  
        $dumpfile("dump.vcd");  
        $dumpvars;  
  
        $display("FA - Full Adder Test Results");  
        $display("-----");  
  
        // Display signal values at every change  
        $monitor("Time=%0t, a=%b, b=%b, cin = %b, sum=%b, carry=%b", $time, net_test_a, net_test_b, net_test_cin,  
            net_test_sum, net_test_cout);  
  
        // Apply 8 input combinations  
        net_test_a = 1'b0; net_test_b = 1'b0; net_test_cin = 1'b0; #10  
        net_test_a = 1'b0; net_test_b = 1'b0; net_test_cin = 1'b1; #10  
  
        net_test_a = 1'b0; net_test_b = 1'b1; net_test_cin = 1'b0; #10  
        net_test_a = 1'b0; net_test_b = 1'b1; net_test_cin = 1'b1; #10  
  
        net_test_a = 1'b1; net_test_b = 1'b0; net_test_cin = 1'b0; #10  
        net_test_a = 1'b1; net_test_b = 1'b0; net_test_cin = 1'b1; #10  
  
        net_test_a = 1'b1; net_test_b = 1'b1; net_test_cin = 1'b0; #10  
        net_test_a = 1'b1; net_test_b = 1'b1; net_test_cin = 1'b1; #10  
    end  
endmodule
```

```


net_test_a = 1'b1; net_test_b = 1'b0; net_test_cin = 1'b0; #10
net_test_a = 1'b1; net_test_b = 1'b0; net_test_cin = 1'b1; #10

net_test_a = 1'b1; net_test_b = 1'b1; net_test_cin = 1'b0; #10
net_test_a = 1'b1; net_test_b = 1'b1; net_test_cin = 1'b1; #10

// End simulation
$finish;
end
endmodule

```

Simulation Result

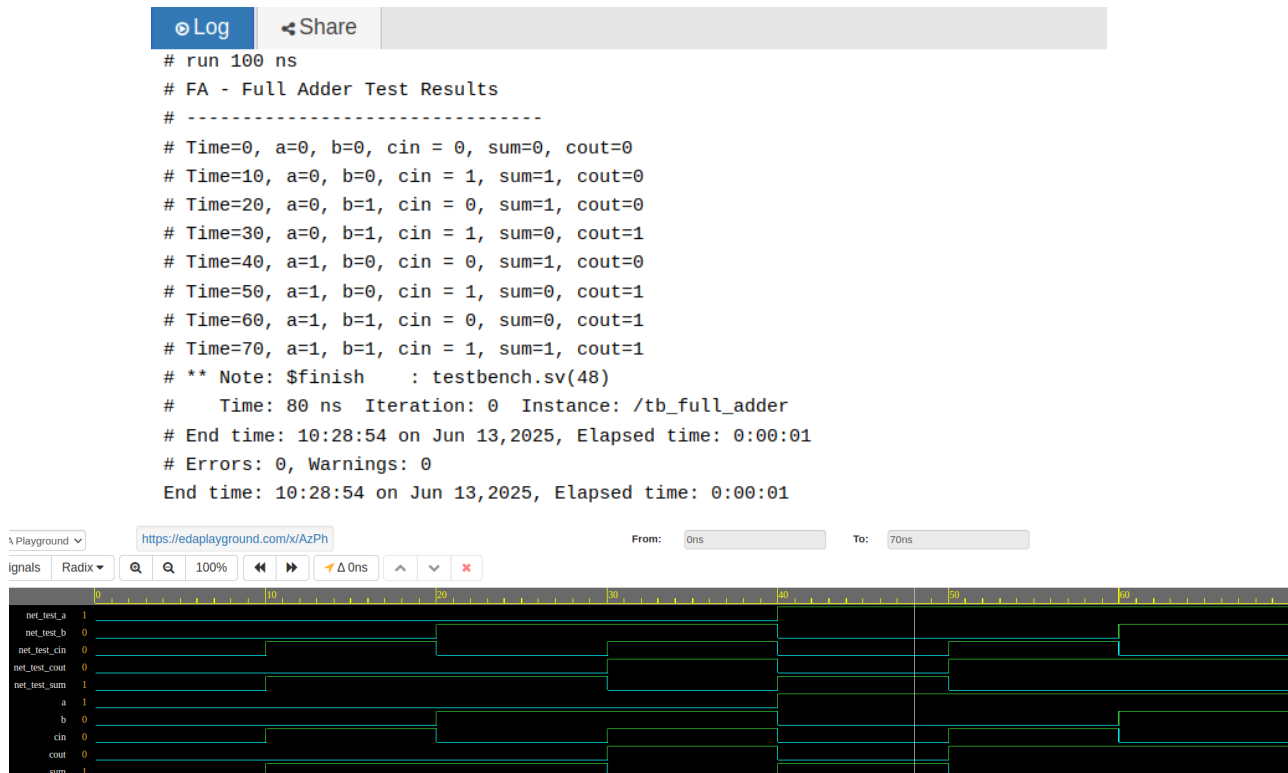

[2. 16-bit full adder]

RTL

```

// =====
// 16-bit Ripple Carry Adder Module
// This parameterized module constructs an N-bit ripple carry adder using N instances of the full_adder module.
// It takes two N-bit inputs (a and b), a carry-in (cin), and produces an N-bit sum and a final carry-out (cout).
// =====
module _16bit_full_adder #(parameter N=16) (a, b, cin, sum, cout);
    input [N-1:0] a, b; // Input: Two N-bit binary numbers (a and b)
    input cin;          // Input: Carry-in bit
    output [N-1:0] sum; // Output: N-bit sum of a and b with carry-in
    output cout;        // Output: Final carry-out bit

    wire [N:0] c;        // Internal carry wires
    assign c[0] = cin;   // Initial carry-in

    genvar i;

```

```

// Generate N full adder instances for each bit
generate
  for (i = 0; i < N ; i = i + 1) begin : gen_fa
    full_adder fa (
      .a(a[i]),
      .b(b[i]),
      .cin(c[i]),
      .sum(sum[i]),
      .cout(c[i+1])
    );
  end
endgenerate

assign cout = c[N]; // Assign final carry-out
endmodule

// =====
// Full Adder Module 2
// This module implements a full adder using two half adder instances,
// taking three 1-bit bin inputs (a, b, cin) and producing a 1-bit sum and cout.
// =====
module full_adder (a,b,cin, sum,cout);
  input a,b,cin;
  output sum,cout;

  assign {cout, sum} = {((a & b) | (b & cin) | (a & cin)), (a ^ b ^ cin)};
endmodule

```

TB

```

// =====
// Testbench for 16-bit Full Adder Module
// This testbench verifies the behavior of the 16bit_full_adder module
// by applying multiple input combinations across 16 bits and monitoring outputs.
// =====
module tb_16bit_full_adder;
  reg [15:0] net_test_a; // Input a for testing: 16-bit first input
  reg [15:0] net_test_b; // Input b for testing: 16-bit second input
  reg net_test_cin; // Input cin for testing: Carry-in bit
  wire [15:0] net_test_sum; // Output sum for testing: 16-bit result of the addition
  wire net_test_cout; // Output cout for testing: Carry-out bit

  // Instantiate 16-bit Full Adder module
  _16bit_full_adder _16b_fa_test (
    .a(net_test_a), // Connect test input a to module input a
    .b(net_test_b), // Connect test input b to module input b
    .cin(net_test_cin), // Connect test input cin to module input cin
    .sum(net_test_sum), // Connect module output sum to test wire
    .cout(net_test_cout) // Connect module output cout to test wire
  );

  // Initial block to perform test cases
  initial begin
    // Create VCD file for waveform analysis
    $dumpfile("dump_16bit.vcd");
    $dumpvars;

    $display("16-bit FA - 16-bit Full Adder Test Results");
    $display("-----");

    // Display signal values at every change

```

```
$monitor("Time=%0t, a=%h, b=%h, cin=%b, sum=%h, cout=%b", $time, net_test_a, net_test_b, net_test_cin, net_test_sum, net_test_cout);
```

```
// Apply multiple input combinations
```

```
net_test_a = 16'h0000; net_test_b = 16'h0000; net_test_cin = 1'b0; #10;  
net_test_a = 16'h0001; net_test_b = 16'h0002; net_test_cin = 1'b1; #10;  
net_test_a = 16'hABCD; net_test_b = 16'hEF01; net_test_cin = 1'b0; #10;  
net_test_a = 16'hFFFF; net_test_b = 16'hFFFF; net_test_cin = 1'b1; #10;  
net_test_a = 16'h1234; net_test_b = 16'h5678; net_test_cin = 1'b0; #10;  
net_test_a = 16'h5555; net_test_b = 16'h5555; net_test_cin = 1'b1; #10;
```

```
// End simulation
```

```
$finish;
```

```
end
```

```
endmodule
```

Simulation Result

Log

Share

```
# run 100 ns  
# 16-bit FA - 16-bit Full Adder Test Results  
# -----  
# Time=0, a=0000, b=0000, cin=0, sum=0000, cout=0  
# Time=10, a=0001, b=0002, cin=1, sum=0004, cout=0  
# Time=20, a=abcd, b=ef01, cin=0, sum=9ace, cout=1  
# Time=30, a=ffff, b=ffff, cin=1, sum=ffff, cout=1  
# Time=40, a=1234, b=5678, cin=0, sum=68ac, cout=0  
# Time=50, a=5555, b=5555, cin=1, sum=aaab, cout=0  
# ** Note: $finish      : testbench.sv(43)  
#   Time: 60 ns  Iteration: 0  Instance: /tb_16bit_full_adder  
# End time: 11:17:23 on Jun 13,2025, Elapsed time: 0:00:01  
# Errors: 0, Warnings: 0  
End time: 11:17:23 on Jun 13,2025, Elapsed time: 0:00:01
```